



Electrical properties of GaN LEDs & Parallel connections

Table of contents

1. Overview	2
2. Parallel Connection of GaN-basis LED	2
3. Summary.....	5

The part number NSCW215 in this document is the part number of Nichia's product, and does not have any relevance or similarity to other companies' products that may have trademark rights.

1. Overview

For reference on current and forward voltage, please consult Nichia's LED Product Guide 2004. In this example, Table 1 provides the forward voltage of NSCW215 as 3.6V (Typ.), 4.0V (Max.) at $I_F=20\text{mA}$. This indicates for a group of LEDs, the forward voltage - forward current characteristic is not a single fixed value. In a group of LEDs operating at 20mA the voltage will be an average of 3.6 volts with a maximum of 4.0 volts. But for any given LED in the group the VF may be any value between 2.8 and 4.0 volts. Therefore, when constructing a system where GaN-basis LEDs are connected in parallel, please note the following conditions.

- Even if you energize the same voltage to the same product, the current can be different.
- If the current value is different, the luminous intensity is also different.
- If the current value is different, the color can also be different.

Table 1. Forward Voltage of NSCW215 ($I_F=20\text{mA}$)

Forward Voltage V_F (V)	
Typ.	Max.
3.6	4.0

2. Parallel Connection of GaN-basis LED

2.1. Example 1 (A circuit with 2 resistors)

Designing following circuit with LEDs under different forward voltage characteristics.

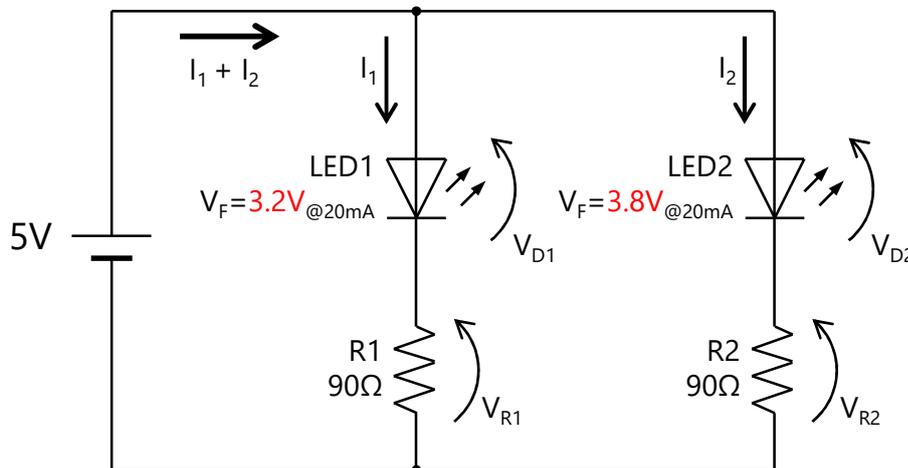


Figure.1: Circuit Diagram

Supposition

Suppose as follows:

Power-supply voltage: 5V

LED1 side: 3.2V at 20mA with 90Ω

LED2 side: 3.8V at 20mA with 90Ω

The current value of I₁ side is calculated as follows.

Postulation#1

$$I_1 = 10\text{mA}$$

$$V_{R1} = 10\text{mA} \times 90 \Omega = 0.9 \text{ V}$$

$$V_{D1} = 5 \text{ V} - 0.9 \text{ V} = 4.1 \text{ V}$$

Refer to Figure 2 which shows: V_F = 3.06V at 10mA

Therefore, V_{D1} should be 3.06V.

As the result, 10mA of Postulation#1 is not correct.

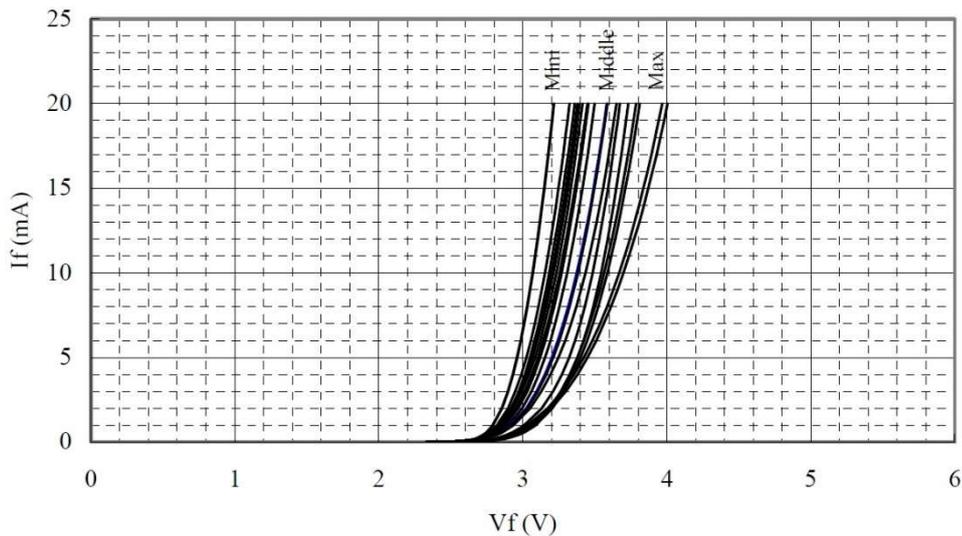


Figure 2. Forward Voltage - Forward Current

Postulation#2

$$I_1 = 15 \text{ mA}$$

$$V_{R1} = 15 \text{ mA} \times 90 \Omega = 1.35 \text{ V}$$

$$V_{D1} = 5 \text{ V} - 1.35 \text{ V} = 3.65 \text{ V}$$

Refer to Figure 2 which shows: V_F = 3.14V at 15mA

Therefore, V_{D1} should be 3.14 V

As the result, Postulation#2 is not correct but the "15mA" is more accurate than "10mA".

Postulation#3

$$I_1 = 20 \text{ mA}$$

$$V_{R1} = 20 \text{ mA} \times 90 \Omega = 1.8 \text{ V}$$

$$V_{D1} = 5 \text{ V} - 1.8 \text{ V} = 3.2 \text{ V}$$

Postulation#3 equal to the "Supposition"

The same way of calculation will result as I₂=15mA.

2.2. Example 2 (A circuit with 1 resistor)

The circuit with one resistance that is cost-effective.

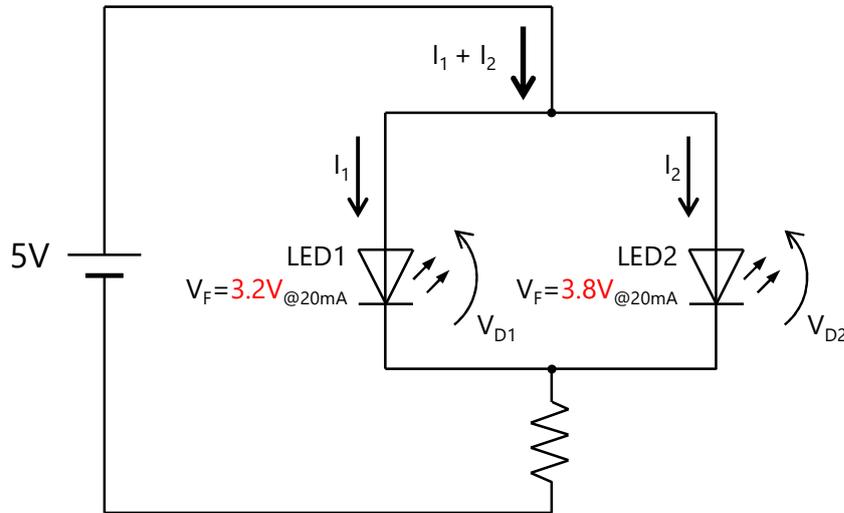


Figure 3. Circuit Diagram

Supposition

Suppose as follows:

Power-supply voltage: 5V

LED1 side: 3.2V at 20mA

LED2 side: 3.8V at 20mA

The current value of I_1 side is calculated as follows.

Postulation#1

$$I_1 = 20 \text{ mA}$$

$$V_{D1} = 3.2 \text{ V}$$

$$V_{D1} = V_{D2}$$

Therefore, $V_{D2} = 3.2 \text{ V}$

The current value of I_2 is 2mA which is derived from Figure 2

Therefore, $I_1:I_2 = 10:1$

Postulation#2

$$I_2 = 20 \text{ mA}$$

$$V_{D2} = 3.8 \text{ V}$$

$$V_{D2} = V_{D1} = 3.8 \text{ V}$$

The current, I_1 , exceeds the scope of the graph of current vs. voltage shown in Figure 2. An LED used in this manner may also exceed Nichia's defined absolute maximum current. The luminous intensity of LED1 compared to LED2 will be noticeably different.

Please refer to Nichia's product specifications for reference on the maximum allowable forward current.

Please do not exceed the absolute maximum current when using Nichia LEDs.

3. Summary

When two LEDs of similar luminous intensity are driven at the same current, they will appear identical. This can be achieved using a parallel connection where both LEDs are at the same forward voltage. However, if the voltage changes the luminous intensity will change according to the forward current change of each LED.

As shown in Figure 1, adjusting the voltage with separate resistors will reduce variation in forward current resulting giving similar luminous intensity values. For the example of Figure 1, both resistors were the same thus the luminous intensity would not be the same. If the resistors were matched to the VF of the LED, the same luminous intensity could be achieved.

Theoretically one could consider very narrow VF binning as a solution. Practically this is not an answer. When the range of available product becomes small, the ability to ship decreases and the cost drastically increases. The best answer in this case is one which considers VF variation as a function of the product and strives to limit its effect on the system.

Disclaimer

This application note is a controlled document of Nichia Corporation (Nichia) published to provide technical information/data for reference purposes only. By using this application note, the user agrees to the following:

- This application note has been prepared solely for reference on the subject matters incorporated within it and Nichia makes no guarantee that customers will see the same results for their chosen application.
- The information/data contained herein are only typical examples of performances and/or applications for the product. Nichia does not provide any guarantees or grant any license under or immunity from any intellectual property rights or other rights held by Nichia or third parties.
- Nichia makes no representation or warranty, express or implied, as to the accuracy, completeness or usefulness of any information contained herein. In addition, Nichia shall not be liable for any damages or losses arising out of exploiting, using, or downloading or otherwise this document, or any other acts associated with this document.
- The content of this application note may be changed without any prior or subsequent notice.
- Copyrights and all other rights regarding the content of this document are reserved by Nichia or the right holders who have permitted Nichia to use the content. Without prior written consent of Nichia, republication, reproduction, and/or redistribution of the content of this document in any form or by any means, whether in whole or in part, including modifications or derivative works hereof, is strictly prohibited.

NICHIA CORPORATION 491 Oka, Kaminaka-Cho, Anan-Shi,
TOKUSHIMA 774-8601, JAPAN

<http://www.nichia.co.jp> Phone: +81-884-22-2311 Fax: +81-884-21-0148